



**R18 Regulation**  
**TKR COLLEGE OF ENGINEERING AND TECHNOLOGY**  
(Autonomous, Accredited by NAAC with 'A' Grade)

Subject code: 2P5BB

## B.Tech V Semester Supplementary Examinations, June 2022

### POWER ELECTRONICS (ELECTRICAL & ELECTRONICS ENGINEERING)

Maximum Marks: 70

Date: 04.07.2022 Duration: 3 hours

- Note:
1. This question paper contains two parts A and B.
  2. Part A is compulsory which carries 20 marks. Answer all questions in Part A.
  3. Part B consists of 5 Units. Answer any one full question from each unit.
  4. Each question carries 10 marks and may have a, b, c, d as sub questions.

#### Part-A

All the following questions carry equal marks

- 1 What is meant by holding current and latching current in SCR? (10x2M=20 Marks)
- 2 Explain in detail various voltage ratings and current ratings of a thyristor.
- 3 Define ripple factor input displacement factor, total harmonic distortion
- 4 What is meant by extinction angle and conduction angle?
- 5 Explain the various control strategies for varying duty cycle.
- 6 Define the ac voltage controllers and give its application.
- 7 Define Load commutation.
- 8 What are the methods of voltage control within the inverter?
- 9 Define the function of inverter and its applications.
- 10 How can a PWM control signal be obtained using a carrier wave and reference wave with the help of diagram.

#### Part-B

Answer All the following questions.

- 11 a) Explain the R firing circuit of SCR. (10M X 5=50Marks) [5M]  
b) Explain the operation of IGBT with VI and switching characteristics. [5M]
- 12 Explain the dynamic turn on and turn off characteristics of SCR? OR [10M]
- 13 Explain the operation of three phase half wave-controlled converter with R-load. OR [10M]
- 14 Explain the operation of single-phase half controlled bridge converter with RL loads. Describe in detail with discontinuous conduction mode with associated waveforms. [10M]
- 15 a) Derive an expression for output voltage of a buck dc-dc converter operating under CCM. [5M]  
b) Obtain the input-output voltage and current relation as a function of duty ratio

for a Buck-Boost dc-dc converter in continuous conduction mode. [5M]

OR

- 16 a) Explain the operation of a single-phase ac voltage controller with R-load and derive all necessary equations. [5M]  
b) For a single-phase AC voltage controller feeding resistance load of 10 ohms. The rms of i/p voltage is 120V at 60Hz. The delay angle of thyristor is  $60^\circ$ . Calculate the value of a). the rms o/p voltage b). Input power factor. [5M]

- 17 a) Explain the operation of single-phase bridge inverter with the help of load voltage and load current waveforms for RL Load. [6M]  
b) Explain the sinusoidal pulse width modulation used in single phase inverter and draw its waveform. [4M]

OR

- 18 A single-phase bridge inverter fed from 200 V dc, is connected to an RL load of  $R = 9 \Omega$  and  $L = 0.04 \text{ H}$ . Determine the power delivered to the load in case the inverter is operating at 50 Hz with square wave output. [10M]

- 19 a) Describe the operation of 3-phase bridge inverter circuit diagram with resistive load in  $120^\circ$  conduction mode. [7M]  
b) Compare voltage source and current source inverters. [3M]

OR

- 20 A 3-phase bridge inverter is operated in  $180^\circ$  conduction mode. Derive output line voltage and phase voltage expression. [10M]