



Regulation R18
TKR COLLEGE OF ENGINEERING AND TECHNOLOGY
(Autonomous, Accredited by NAAC with 'A' Grade)

Subject code: 2E7BC

B.Tech VII Semester Supplementary Examinations, July 2022

FLEXIBLE AC TRANSMISSION SYSTEMS (ELECTRICAL AND ELECTRONICS ENGINEERING)

Maximum Marks: 70

Date:04.07.2022 Duration: 3 hours

- Note: 1. This question paper contains two parts A and B.
2. Part A is compulsory which carries 20 marks. Answer all questions in Part A.
3. Part B consists of 5 Units. Answer any one full question from each unit.
4. Each question carries 10 marks and may have a, b, c, d as sub questions.

Part-A

All the following questions carry equal marks

(10x2M=20 Marks)

- 1 What are the objectives of FACTS controllers?
- 2 Why in general voltage sourced converters is preferred over current sourced converters in FACTS controllers?
- 3 Write the three important objectives of shunt compensation.
- 4 What are the characteristics differences between TSSC and TCSC?
- 5 What is reactive power? What is its significance?
- 6 What are the advantages of thyristor switched capacitors?
- 7 What are the objectives of series compensation?
- 8 Explain different losses that are encountered with FC – TCR arrangement.
- 9 Explain main objectives and usefulness of UPFC in power industry
- 10 List merits of Hybrid compensator.

Part-B

Answer All the following questions.

(10M X 5=50Marks)

- 11 a) Explain various loading capability limits in power flow systems. [5]
b) Enumerate single phase full-wave bridge Voltage Source Converter operation. [5]

OR

- 12 a) Explain prevention of voltage stability with the help of end of line voltage support? [5]
b) Explain all Shunt Connected Controllers with neat diagram? [5]
- 13 Explain the Switching converter type VAR Generator? [10]

OR

- 14 a) Explain the improvement of transient stability? [5]
b) What is the need for reactive power compensation in transmission systems? [5]

15 With a neat circuit diagram and necessary waveforms, discuss the operation of a Thyristor Controlled Reactor (TCR). Also represent their V-I operating area. [10]

OR

16 Explain the operation of STATCOM with an aid of block diagram. [10]

17 Explain the voltage stability enhancement and power oscillation damping with series capacitive compensation. [10]

OR

18 Explain with a neat sketch and waveforms the GCSC type of series controller. [10]

19 Explain the implementation of the UPFC by back-to-back voltage sourced converters. [10]

OR

20 What is interline power flow controller? With a schematic diagram, explain its working. [10]