



**FLEXIBLE AC TRANSMISSION SYSTEMS**  
**(EEE)**

**Maximum Marks: 70**

**Date: 12.12.2023 Duration: 3 hours**

- Note:**
1. This question paper contains two parts A and B.
  2. Part A is compulsory which carries 20 marks. Answer all questions in Part A.
  3. Part B consists of 5 Units. Answer any one full question from each unit which carries 10M.
  4. Each question carries 10 marks and may have a, b, c, d as sub questions.

**Part-A**

All the following questions carry equal marks

(10x2M=20 Marks)

Bloom

1	What are the objectives of FACTS controllers?		Tx
2	What are the basic types of FACTS controllers?		L1
3	How shunt compensation is classified?		L1
4	What are the characteristics differences between TSSC and TCSC?		L1
5	What are the advantages of slope in SVC dynamic characteristics?		L1
6	What are the advantages of thyristor switched capacitors?		L1
7	What are the functions of STATCOM in the improvement of power system performance area?		L1
8	What are the conventional methods used for compensation in power systems?		L1
9	What is a stand-alone series compensation?		L1
10	List merits of Hybrid compensator.		L1

**Part-B**

Answer All the following questions.

(5X10M=50Marks)

11	Why electrical transmission systems are interconnected? Explain. [10]		L2
	OR		
12	What are voltage sourced converters? Why voltage sourced converters are preferred for FACTS application. [10]		L2
13	Explain the Switching converter type VAR Generator. [10]		L2
	OR		
14	Write short note on [3+3+4] 1) Thermal capability 2) Dielectric capability 3) Stability limit		L2
15	With a neat circuit diagram and necessary waveforms, discuss the operation of a Thyristor Controlled Reactor (TCR). Also represent their V-I operating area. [10]		L3
	OR		

16	Emphasize features of thyristor-controlled reactor. [10]	L3
17	Explain the voltage stability enhancement and power oscillation damping with series capacitive compensation. [10]	L2
	OR	
18	Describe the transfer function and dynamic performance of SVC and STATCOM with necessary diagrams. [10]	L4
19	Explain the implementation of the UPFC by back-to-back voltage sourced converters. [10]	L2
	OR	
20	Write a comparison between IPFC and UPFC. [10]	L3