



R18 Regulation

Subject code: 2P4BB

**TKR COLLEGE OF ENGINEERING AND TECHNOLOGY**

(Autonomous, Accredited by NAAC with 'A' Grade)

**B.Tech IV Semester Supplementary Examinations, September 2023**

### Digital Logical Design

(EEE)

**Maximum Marks: 70**

**Date: 24.09.2023 Duration: 3 hours**

- Note:
1. This question paper contains two parts A and B.
  2. Part A is compulsory which carries 20 marks. Answer all questions in Part A.
  3. Part B consists of 5 Units. Answer any one full question from each unit.
  4. Each question carries 10 marks and may have a, b, c, d as sub questions.

#### Part-A

All the following questions carry equal marks

(10x2M=20 Marks)

- 1 What is Gray code?
- 2 What are the different illegal states of BCD and XS-3?
- 3 What is maxterms? Give example.
- 4 Why is minimization of switching functions required.
- 5 Compare combinational and sequential circuits.
- 6 List the applications of Multiplexers
- 7 Differentiate between RAM and ROM.
- 8 What are drawbacks of ripple counters?
- 9 What is merger graph?
- 10 Define sequential machine.

#### Part-B

Answer All the following questions.

(5X10M=50Marks)

- 11 a) Given the 8 bit data word 11011011, generate the 12 bit composite word for the Hamming code that corrects and detects single errors. (5M)  
b) Convert  $(A0F9.0DC)_{16}$  to decimal, binary, octal (5M)  
OR
- 12 Expand  $(A+D')(A+C')(A'+B)(A'+B+C)$  into max terms and min terms. (10M)
- 13 Minimize the following expression using K-map and realize using NAND Gates.  
 $F(A,B,C,D) = \sum m(0,1,2,9,11) + d(8,10,14,15)$ . (10M)  
OR
- 14 Explain about Multiplexer. Design a 32X1 multiplexer using 4x1 multiplexer. (10M)
- 15 Explain the priority encoder with a neat logic diagram. (10M)  
OR
- 16 What is meant by Edge triggered? Differentiate SR-FF and JK-FF with their functional operation and excitation tables. (10M)
- 17 Design a synchronous 3-bit Up-down counter using JK FFs. (10M)  
OR
- 18 Design a 4-bit up/down Synchronous BCD counter using T flip flops. (10M)
- 19 Explain about sequential circuits, state table and state diagram (10M)  
OR
- 20 Explain about Mealy machine with circuit diagram. (10M)

