



R22 Regulation

Subject code: 4E1AE

TKR COLLEGE OF ENGINEERING AND TECHNOLOGY

(Autonomous, Accredited by NAAC with 'A+' Grade)

B.Tech I Semester Regular/Supplementary Examinations, January 2024

Electrical Circuits

(EEE)

Maximum Marks: 60

Date: 27.01.2024 Duration: 3 hours

- Note:
1. This question paper contains two parts A and B.
 2. Part A is compulsory which carries 10 marks. Answer all questions in Part A.
 3. Part B consists of 5 Units. Answer any one full question from each unit.
 4. Each question carries 10 marks and may have a, b, c, d as sub questions.

Part-A

All the following questions carry equal marks


(10x1M=10 Marks)

			CO	Bloom Tx
1.	a	Write the expression for voltage across inductor and current through capacitor	1	BL1
	b	Two capacitors with capacitances of 3F and 6F are connected in series. Determine the equivalent capacitance	1	BL3
	c	A sinusoidal source is represented by $v(t)=300\sin 314t$. Determine the RMS value and time period of the waveform.	2	BL3
	d	Define power factor.	2	BL4
	e	Write the statement of Tellegen's theorem.	3	BL4
	f	An ac circuit with source impedance of $6+j8\ \Omega$ delivers power to load. Determine the value of load impedance for maximum power transfer to the load.	3	BL3
	g	Write the advantages of three-phase systems over single phase systems.	4	BL2
	h	Write the significance of phase sequence.	4	BL4
	i	What is planar network. Define twig	5	BL1
	j	Define mutual inductance	5	BL1

Part-B

Answer All the following questions.

(5X10M=50Marks)

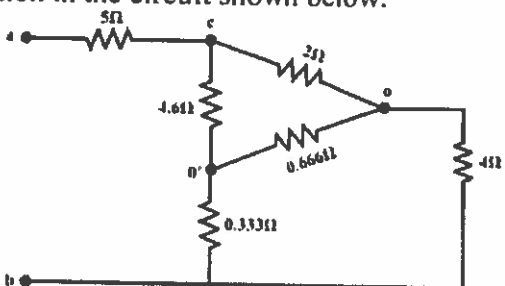2	a) State and explain Kirchhoff's laws. b) Compare Mesh and Nodal analysis with suitable examples. [5+5]	1	BL3
OR			
3	a) Differentiate active and passive elements with examples. b) Determine the resistance between the terminals a and b using star-delta transformation in the circuit shown below. 	1	BL2

[5+5]

4	<p>a) Determine the formfactor of half wave rectified sinusoidal voltage waveform.</p> <p>b) A series RLC circuit with $R=20\Omega$, $L=0.1\text{H}$ and $C=50\mu\text{F}$ is excited by single phase 230V, 50Hz ac source. Determine</p> <p>(i) Impedance of the circuit</p> <p>(ii) Current</p> <p>(iii) Power and</p> <p>(iv) Power factor of the load [5+5]</p>	2	BL4
	OR		
5	<p>a) What are locus diagrams. Write few applications of locus diagrams.</p> <p>b) Derive an expression for band width of a series RLC circuit. [5+5]</p>	2	BL1
6	State and prove superposition theorem with suitable example. [10]	3	BL2
	OR		
7	State and prove maximum power transfer theorem with suitable example. [10]	3	BL4
8	Prove that two watt meters are sufficient to measure the total 3-phase active power in a 3-phase circuit. Write the advantages of two watt meter method over three watt meter method. [10]	4	BL2
	OR		
9	What is star and delta balance load. Prove that current in the neutral wire of a three phase 4 wire balanced star connected system is zero. [10]	4	BL4
10	<p>a) Define co-efficient of coupling. Derive an expression for it.</p> <p>b) Compare magnetic and electrical circuits. [5+5]</p>	5	BL3
	OR		
11	<p>a) What is incidence matrix. Write the properties of incidence matrix.</p> <p>b) Determine the tie-set matrix for the graph shown in figure. Consider the branch of tree as b, c and e. [5+5]</p>	5	BL4

