



**R22 Regulation**  
**TKR COLLEGE OF ENGINEERING AND TECHNOLOGY**  
 (Autonomous, Accredited by NAAC with 'A+' Grade)

Subject code: 4E1AI

**B.Tech I Semester Regular/Supplementary Examinations, January 2024**

**FUNDAMENTALS OF ELECTRICAL ENGINEERING**  
**(ELECTRONICS & COMMUNICATION ENGINEERING)**

**Maximum Marks: 60**

Date: 20.01.2024 Duration: 3 hours

- Note:**
1. This question paper contains two parts A and B.
  2. Part A is compulsory which carries 10 marks. Answer all questions in Part A.
  3. Part B consists of 5 Units. Answer any one full question from each unit.
  4. Each question carries 10 marks and may have a, b, c, d as sub questions.

**Part-A**

All the following questions carry equal marks (10x1M=10 Marks)			CO No.	Bloom Tx
1.	a	State the steps in Nodal analysis.	CO1	BL1
	b	What are the types of dependent sources.	CO1	BL1
	c	Draw the response of Series RC circuit for step input.	CO1	BL2
	d	Define RMS value.	CO1	BL1
	e	Write the principle of Transformer.	CO2	BL1
	f	What is the difference between Electric circuit and Magnetic circuit.	CO2	BL2
	g	What are the types of Armature windings in DC Machine.	CO3	BL2
	h	State the Principle of DC Motor.	CO3	BL1
	i	What is MCCB.	CO4	BL1
	j	State the function of SFU.	CO4	BL1

**Part-B**

Answer All the following questions. (5X10M=50Marks)				
2	A. State and explain Krichoff's laws with an example. [5M]		CO1	BL2
	B. Find $I_o$ using mesh analysis for circuit shown below. [5M]		CO1	BL4
<p style="text-align: center;">Fig. 1</p>				

	OR		
3	A. Explain Star-Delta Transformations and derive expressions for equivalent resistances. [7M]	CO1	BL3
	B. State Superposition theorem. [3M]	CO1	BL2
4	A. Analyze Series RL Circuit for any standard input and derive the expressions for voltage and current. [5M]	CO1	BL3
	B. Illustrate Rectangular and polar representation of phasors. [5M]	CO1	BL2
	OR		
5	A series RLC circuit consists of a resistance of $1K\Omega$ and an inductance of $100mH$ in series with capacitance of $10\mu F$ . If $100 V$ , $50 Hz$ voltage is applied as input across the combination determine total current and voltage across each element in the circuit. [10M]	CO1	BL4
6	A. Explain the principle of working of single-phase transformer on no load conditions. [5M]	CO2	BL3
	B. Draw and explain the Equivalent Circuit of a Transformer on no-load. [5M]	CO2	BL3
	OR		
7	Illustrate the conduction of OC test on 1-phase Transformer with its circuit. [10M]	CO2	BL4
8	Explain the Construction and working principle of DC machines with its diagram. [10M]	CO3	BL3
	OR		
9	Derive an expression for torque developed in a DC motor. [10M]	CO3	BL4
10	A. Explain the Basic concept of wiring systems. [5M]	CO4	BL2
	B. Illustrate power factor improvement methods. [5M]	CO4	BL3
	OR		
11	A. Explain types of Batteries. [5M]	CO4	BL3
	B. Describe the concept of Earthing. [5M]	CO4	BL3